

Primer implementacije CPE v vezju FPGA

- CPE lahko implementiramo (tudi) v programirljivem digitalnem vezju FPGA (Field-Programmable Gate Array)
 - Komercialni procesorji so sicer implementirani v tehnologiji ASIC (Application-Specific Integrated Circuits), ki pa ni lahko dostopna
- FPGA sestavlja polje celic CLB (Configurable logic block) s povezavami
 - oboje uporabnik lahko določi ('programira')


 


Figure 2-1: Basic FPGA Architecture

Primer preproste demo ploščice:

 

CLB vsebuje vpogledno tabelo (LUT) in D flip-flop

- LUT lahko implementira poljubno logično funkcijo 4-6 spremenljivk

Vse slike so iz: Introduction to FPGA Design with VivadoHigh-Level Synthesis. UG998 (v1.1) January 22, 2019, Xilinx.

The hardware implementation of a LUT can be thought of as a collection of memory cells connected to a set of multiplexers. The inputs to the LUT act as selector bits on the multiplexer to select the result at a given point in time. It is important to keep this representation in mind, because a LUT can be used as both a function compute engine and a data storage element. [Figure 2-3](#) shows this functional representation of the LUT.

 


Figure 2-3: Functional Representation of a LUT as Collection of Memory Cells

 


Figure 2-4: Structure of a Flip-Flop

 


Figure 2-2: Contemporary FPGA Architecture

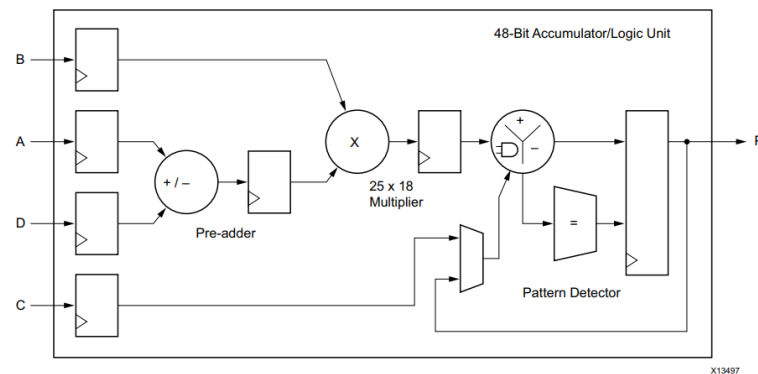


Figure 2-5: Structure of a DSP Block

Primer: Večcikelna CPE (poenostavljen RISC-V iz poglavja 6-CPE)

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;


entity Computer is
    Port (
        reset: in std_logic;
        clock: in std_logic;
        done: out std_logic);
end Computer;

architecture Behavioral of Computer is
    component CPU is
        port (reset: in std_logic;
            clock: in std_logic;
            MemWrite: inout std_logic;
            Adr: out std_logic_vector(31 downto 0);
            ReadData: in std_logic_vector(31 downto 0);
            WriteData: out std_logic_vector(31 downto 0);
            done: out std_logic);
    end component;

    component GP is
        port (reset: in std_logic;
            clock: in std_logic;
            WE: in std_logic;
            A : in std_logic_vector(31 downto 0);
            RD : out std_logic_vector(31 downto 0);
            WD : in std_logic_vector(31 downto 0);
            );
    end component;

    signal MemWrite: std_logic := '0';
    signal A : std_logic_vector(31 downto 0) := (others => '0');
    signal ReadData : std_logic_vector(31 downto 0) := (others => '0');
    signal WriteData : std_logic_vector(31 downto 0) := (others => '0');
    begin
        cpul: CPU port map( reset => reset, clock => clock, MemWrite => MemWrite,
            Adr => A, ReadData => ReadData, WriteData => WriteData, done => done);
        gp1: GP port map( reset => reset, clock => clock, WE => MemWrite,
            A => A, RD => ReadData, WD => WriteData);
    end Behavioral;

```

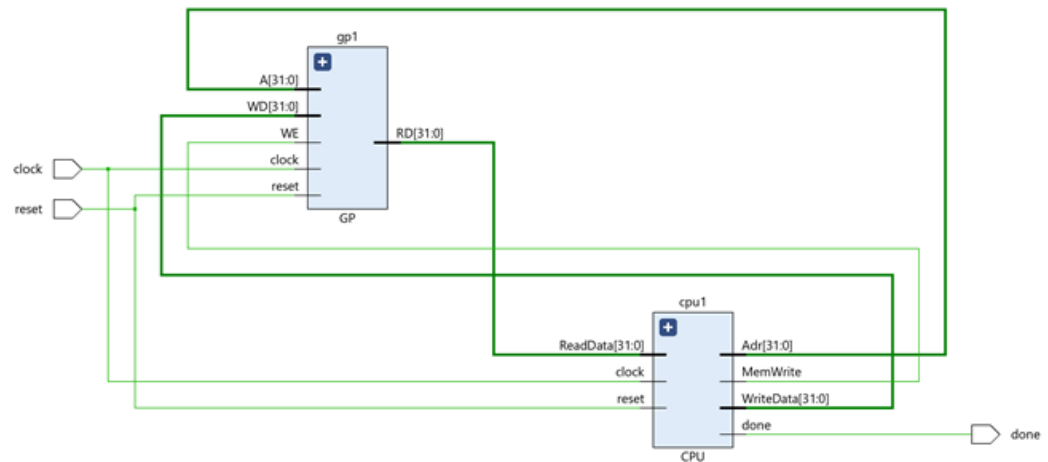

CPE (1. del)

```
entity CPU is
  port (
    reset: in std_logic;
    clock: in std_logic;
    MemWrite: out std_logic;
    Adr: out std_logic_vector(31 downto 0);
    ReadData: in std_logic_vector(31 downto 0);
    WriteData: out std_logic_vector(31 downto 0);
    done: out std_logic
  );
end entity CPU;

architecture top of CPU is
  component KE is...
  component ALU is...

  type RF_array is array (0 to 31) of std_logic_vector(31 downto 0);
  signal RF: RF_array := (others => (others => '0'));

  signal op: std_logic_vector(6 downto 0) := (others => '0');
  signal funct3: std_logic_vector(2 downto 0) := (others => '0');
  signal funct7_5: std_logic := '0';
  signal Zero: std_logic := '0';
  signal PCWrite: std_logic := '0';
  signal IRWrite: std_logic := '0';
  signal AddrSrc: std_logic := '0';
  signal ResultSrc: std_logic_vector(1 downto 0) := (others => '0');
  signal ALUControl: std_logic_vector(2 downto 0) := (others => '0');
  signal ALUSrcB: std_logic_vector(1 downto 0) := (others => '0');
  signal ALUSrcA: std_logic_vector(1 downto 0) := (others => '0');
  signal ImmSrc: std_logic_vector(1 downto 0) := (others => '0');
  signal RegWrite: std_logic := '0';

  signal PC, OldPC: std_logic_vector(31 downto 0) := (others => '0');
  signal IR: std_logic_vector(31 downto 0) := (others => '0');
  signal srcA, srcB: std_logic_vector(31 downto 0) := (others => '0');
```

```
begin

muxAdr: Adr <= PC when AddrSrc = '0' else Result;

procPC: process (clock, reset) is
begin
  if reset = '1' then
    PC <= (others => '0');
  elsif rising_edge(clock) then
    if PCWrite = '1' then
      PC <= Result;
    end if;
  end if;
end process;

procIR: process (clock, reset) is
begin
  if reset = '1' then
    IR <= (others => '0');
    OldPC <= (others => '0');
  elsif rising_edge(clock) then
    if IRWrite = '1' then
      IR <= ReadData;
      OldPC <= PC;
    end if;
  end if;
end process;

procData: process (clock, reset) is
begin
  if reset = '1' then
    Data <= (others => '0');
  elsif rising_edge(clock) then
    Data <= ReadData;
  end if;
end process;

op <= IR(6 downto 0);
```

CPE (2. del)

```
op <= IR(6 downto 0);
funct3 <= IR(14 downto 12);
funct7_5 <= IR(30);

Rs1 <= IR(19 downto 15);
Rs2 <= IR(24 downto 20);
Rd <= IR(11 downto 7);

) procKE: KE port map( reset => reset, clock => clock, op => op, funct3 => funct3,
    funct7_5 => funct7_5, Zero => Zero, PCWrite => PCWrite, MemWrite => MemWrite,
    IRWrite => IRWrite, AdrSrc => AdrSrc, ResultSrc => ResultSrc,
    ALUControl => ALUControl, ALUSrcB => ALUSrcB, ALUSrcA => ALUSrcA,
    ImmSrc => ImmSrc, RegWrite => RegWrite, done => done);

) procRFWrite: process( reset, clock)
begin
    if reset = '1' then
        RF <= (others => (others => '0'));
    elsif rising_edge(clock) then
        if RegWrite = '1' then
            RF(to_integer(unsigned(Rd))) <= Result; --WD3
        end if;
    end if;
end process;

) procRFRead: process( Rs1, Rs2)
begin
    RD1 <= RF(to_integer(unsigned(Rs1)));
    RD2 <= RF(to_integer(unsigned(Rs2)));
end process;

Imm12 <= IR(31 downto 20) when ImmSrc = "00" --IW
    else (IR(31 downto 25) & IR(11 downto 7)) when ImmSrc = "01" --SW
    else (IR(31) & IR(7) & IR(30 downto 25) & IR(11 downto 8)) when ImmSrc = "10" --beq
    else (others => '0');

ImmExt <= (std_logic_vector(to_unsigned(0,20)) & Imm12) when Imm12(11) = '0'
    else (std_logic_vector(to_unsigned(1,20)) & Imm12) when Imm12(11) = '1'
    else std_logic_vector(to_unsigned(0,32));

procRegAB: process( reset, clock)
begin
    if reset = '1' then
        regA <= (others => '0');
        regB <= (others => '0');
    elsif rising_edge(clock) then
        regA <= RD1;
        regB <= RD2;
    end if;
end process;
WriteData <= regB;

srcA <= PC when ALUSrcA = "00" else OldPC when ALUSrcA = "01"
    else regA when ALUSrcA = "10";
srcB <= regB when ALUSrcB = "00" else ImmExt when ALUSrcB = "01"
    else std_logic_vector(to_unsigned(4,32)) when ALUSrcB = "10";

procALU: ALU port map( ALUControl => ALUControl, srcA => srcA, srcB => srcB,
    ALUResult => ALUResult, Zero => Zero);

procALUOut: process (clock, reset) is
begin
    if reset = '1' then
        ALUOut <= (others => '0');
    elsif rising_edge(clock) then
        ALUOut <= ALUResult;
    end if;
end process;

Result <= ALUOut when ResultSrc = "00"
    else Data when ResultSrc = "01"
    else ALUResult when ResultSrc = "10";
end architecture top;
```

Kontrolna enota (KE) je podvezje CPE

- njen glavni del je končni avtomat (FSM), ki ustreza diagramu prehajanja stanj v pog. 6

```
library ieee;
use ieee.std_logic_1164.all, ieee.numeric_std.all;

entity KE is
  port (
    reset: in std_logic;
    clock: in std_logic;
    op: in std_logic_vector(6 downto 0);
    funct3: in std_logic_vector(2 downto 0);
    funct7_5: in std_logic;
    Zero: in std_logic;
    PCWrite: out std_logic;
    MemWrite: out std_logic;
    IRWrite: out std_logic;
    AddrSrc: out std_logic;
    ResultSrc: out std_logic_vector(1 downto 0);
    ALUControl: out std_logic_vector(2 downto 0);
    ALUSrcB: out std_logic_vector(1 downto 0);
    ALUSrcA: out std_logic_vector(1 downto 0);
    ImmSrc: out std_logic_vector(1 downto 0);
    RegWrite: out std_logic;
    done: out std_logic
  );
end KE;

architecture rtl of KE is
  type state_type is (Sr, S0, S1, S2, S3, S4, S5, S6, S7, S10, Serr);
  signal st, nst: state_type;
  signal ALUOp: std_logic_vector(1 downto 0) := (others => '0');
  signal Branch: std_logic := '0';
  signal PCUpdate: std_logic := '0';
begin
  PCWrite <= (Zero and Branch) or PCUpdate;

  InstrDecoder:
    ImmSrc <= "00" when op = "0000011"
    else "01" when op = "0100011"
    else "10" when op = "1100011"
    else "11";

  ALUDecoder:
    <
```

```
when S2 => -- MemAdr
  ALUSrcA <= "10";
  ALUSrcB <= "01";
  ALUOp <= "00";
  if op = "0000011" then -- lw
    nst <= S3;
  elsif op = "0100011" then -- sw
    nst <= S5;
  else
    nst <= Serr;
  end if;

when S3 => -- MemRead
  ResultSrc <= "00";
  AddrSrc <= '1';
  nst <= S4;



when S4 => -- MemWB
  ResultSrc <= "01";
  RegWrite <= '1';
  nst <= S0;

when S5 => -- MemWrite
  ResultSrc <= "00";
  AddrSrc <= '1';
  MemWrite <= '1';
  nst <= S0;

when S6 => -- Execute R
  ALUSrcA <= "10";
  ALUSrcB <= "00";
  ALUOp <= "10";
  nst <= S7;

when S7 => -- ALUWB
  ResultSrc <= "00";
  RegWrite <= '1';
  nst <= S0;
```

Shema KE in ALE:

 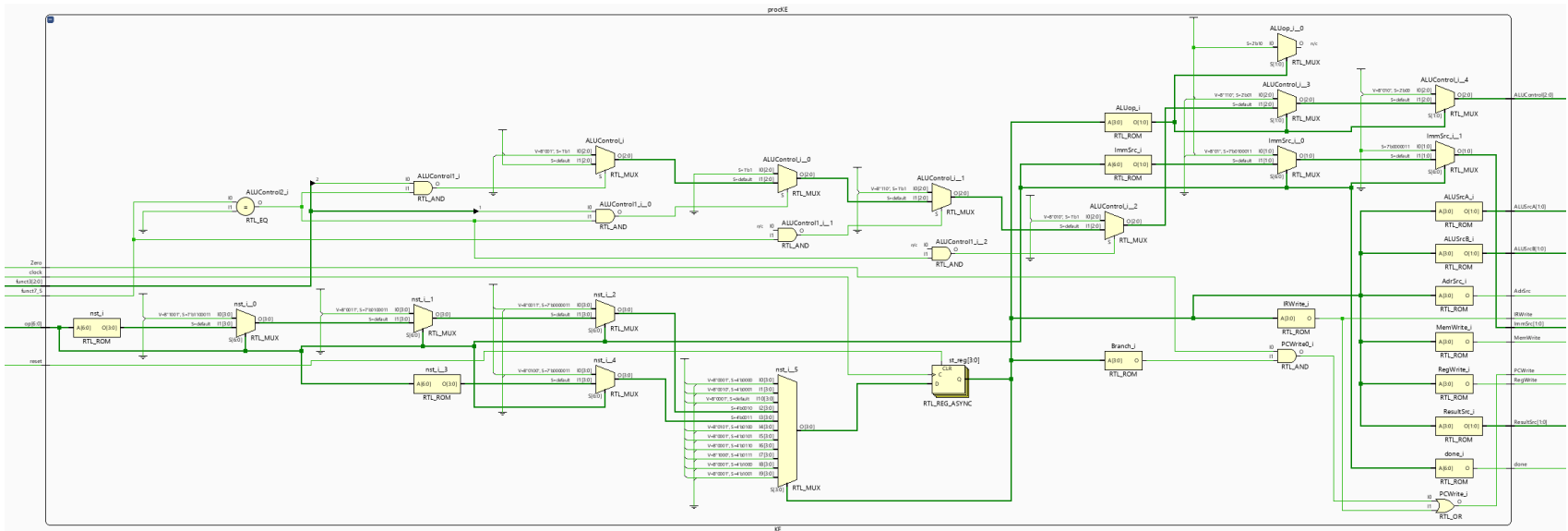

[illegible]

- HDL-jeziki (Hardware Description Language – jezik za opis hardvera):
 - VHDL
 - Verilog
- 2 načina modeliranja v HDL-jeziku:
 - RTL: register transfer level
 - tudi v našem primeru
 - Gate-level
- Postopek implementacije vezja v FPGA:
 - Sinteza
 - Program za sintezo iz opisa v HDL-jeziku sklepa, kakšno vezje želimo implementirati
 - Mapiranje
 - Preslikava elementov vezja v elemente v FPGA (CLB, LUT, FF, BRAM, itd.)
 - Razmestitev in povezovanje (placement, routing)
 - vpliva na zakasnitve in posledično največjo možno frekvenco delovanja
 - Datoteka 'bitstream' se naloži v FPGA
 - celice, ki se jih programira, so tipa SRAM (določajo vsebine tabel LUT, konfiguracijo elementov in povezave v FPGA)

Testiranje (Simulacija)

- funkcionalno (v tej fazi se ne upošteva dejanskih zakasnitev)
- časovno (upošteva izračunane zakasnitve)

Testna VHDL datoteka (Testbench file) podaja potek vhodnih signalov:

```
library ieee;
use ieee.std_logic_1164.all;

entity testComputer is
end entity testComputer;

architecture tb of testComputer is
  component Computer is
    Port ( reset: in std_logic;
          clock: in std_logic;
          done: out std_logic);
  end component Computer;
  constant clk_period: time := 10 ns;
  signal reset: std_logic := '0';
  signal clock: std_logic := '0';
  signal done: std_logic := '0';

  begin
    compl: Computer port map (reset => reset, clock => clock, done => done);

    clk_process: process
    begin
      clock <= not clock;
      wait for clk_period/2;
    end process;

    stim_process: process
    begin
      reset <= '1';
      wait for 1.5*clk_period;
      reset <= '0';
      wait for 25*clk_period;
      wait until done = '0';
      report "Test Done." severity failure;
      assert (FALSE) report "End of simulation." severity Failure;
    end process;
  end architecture tb;
```

Rezultat simulacije, prikazan grafično:

